



An-Najah National University

Faculty of Engineering And Information Technology

Digital Electronic Circuits

(**10636332**)

Homework **3** : Conversion Systems

Instructor: Sulieman Abu Kharmeh

| <i>Name</i> | <i>No.</i> | <i>Participation %</i> |
|-----------------------------------|-----------------|------------------------|
| <i>Ezz Addin Helal Kukhun</i> | <i>11820706</i> | <i>50%</i> |
| <i>Osama Ismael</i> | <i>11821494</i> | <i>50%</i> |

Important Notes:

- *V output 3 : Most Significant Bit.
V output 0 : Least Significant Bit.*
- *NOTE: To Run Homework Correctly , put the XOR (2-bit) file in **Sym Folder in LTSpice.***


ADC Design

In this Assignment , we will demonstrate 4 Bit ADC , so to built this ADC we will use Op-Amp 's , and we will use XOR , and the Amplitude of Input voltage is 100 mV (summation of last two digits of our student number) , and the offset will be $100 / 2 = 50\text{mV}$.


Design :

Firstly , we used 15 Op-Amp 's , because the result will be from 1-15 , and we used Another 4 Op-Amp 's on the output , so total used Op-Amp 's will be 19.

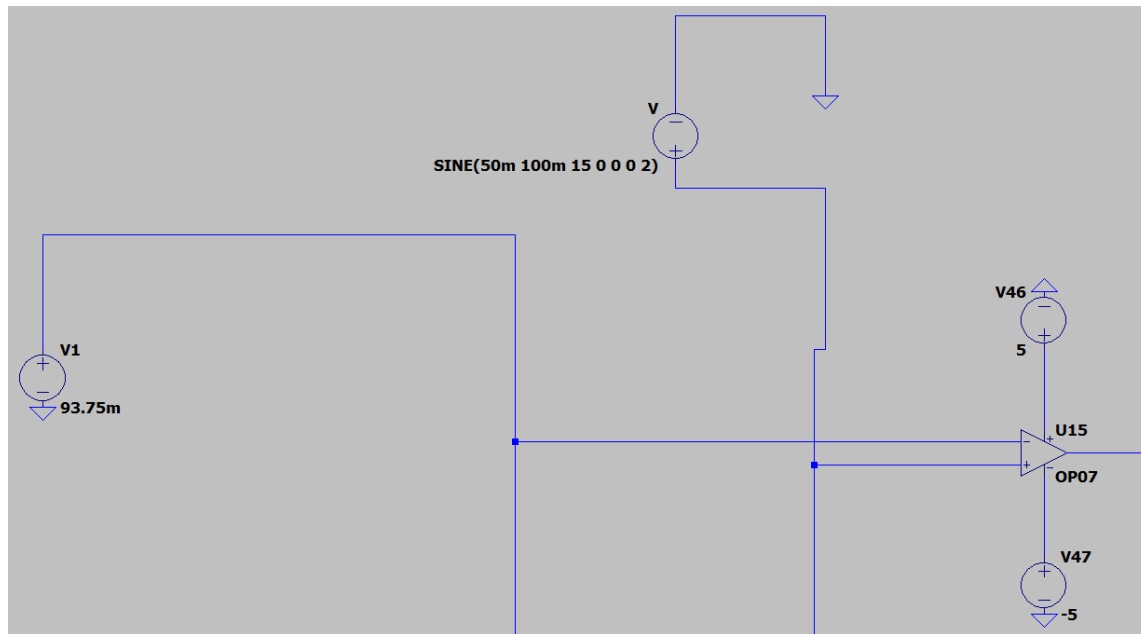
*VCC of Op-Amp $\equiv 5$, and $-VCC = -5$, and we connect the negative terminal Of each Op-Amp with $(15/16)*100\text{mV}$ which is equal 93.75mV , and we connect The positive terminal with sin wave which has amplitude equal 100mV .*



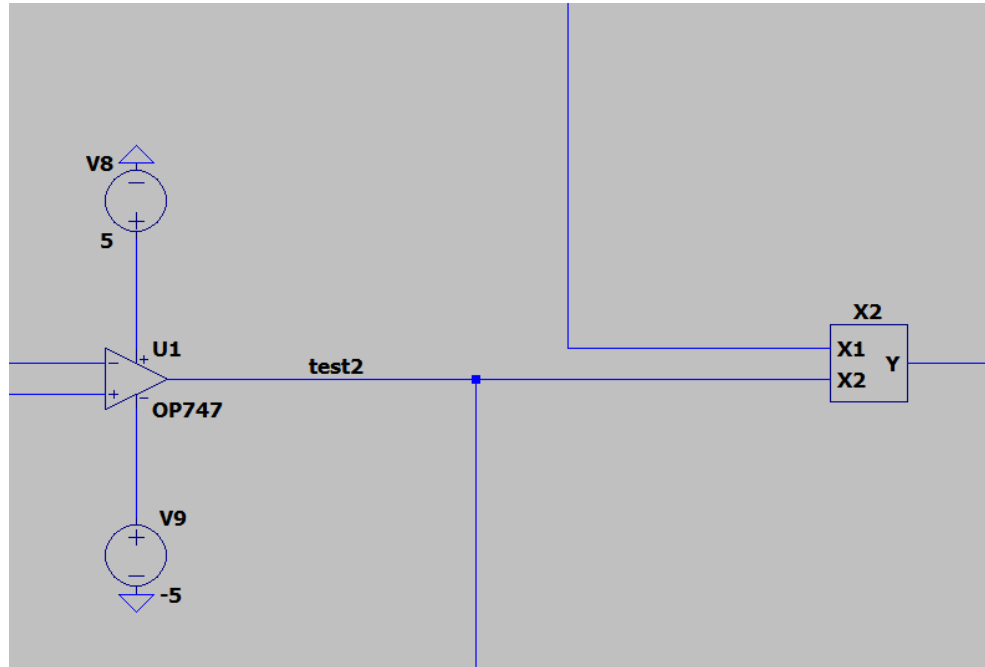Then , we used XOR with 2-Bit input and we built it by transmission gate to Reduce numbers of transistors , any one of inputs of XOR is the result of current Op-amp , and the other input of XOR is the result of previous op-Amp.




XOR Design:

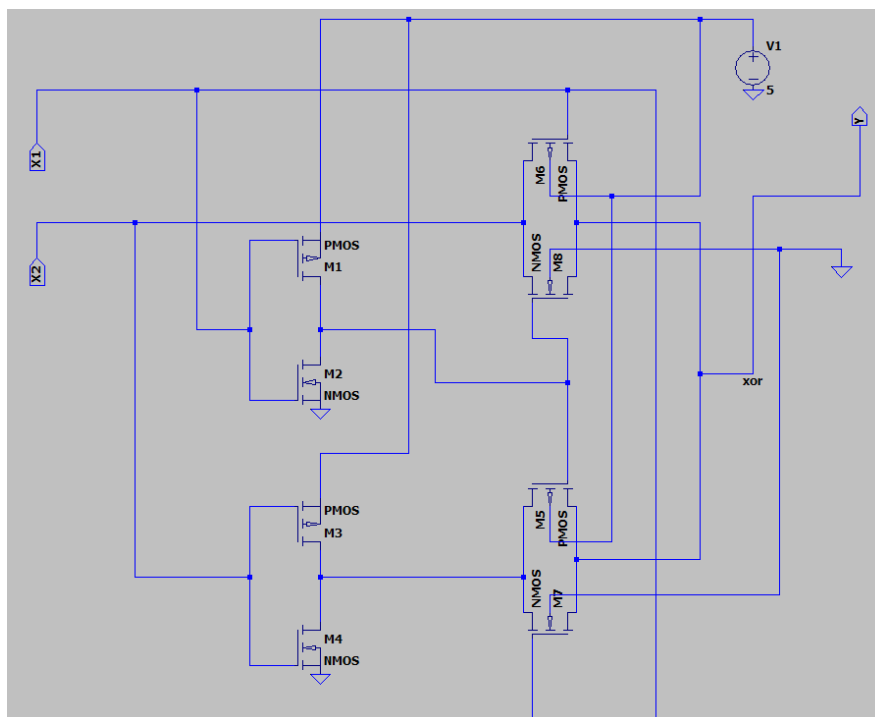


Then, we connected the output of XOR with Diodes , and the number of Diodes Depend on binary number , so if I would represent 0010 , I will use 1 diode , And if I would represent 1101 , I will use 3 diodes , and connect the results Of diodes base on arrange of one's .


Note : this represent 1110

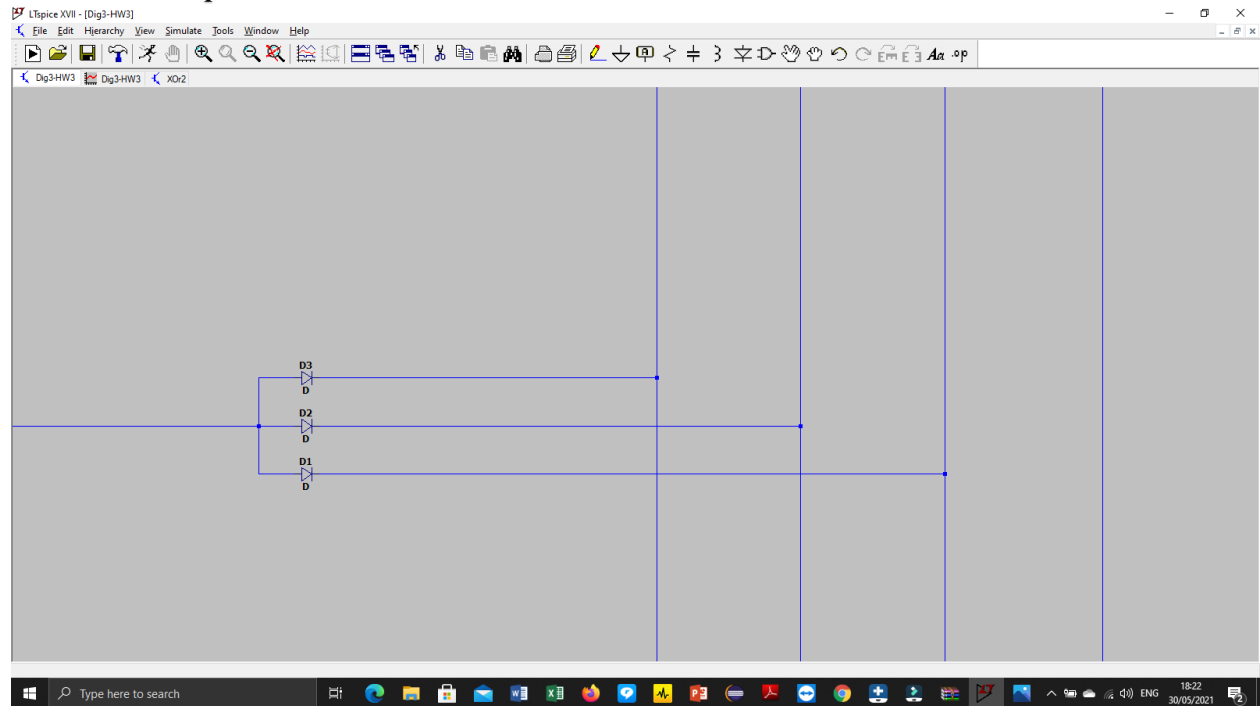

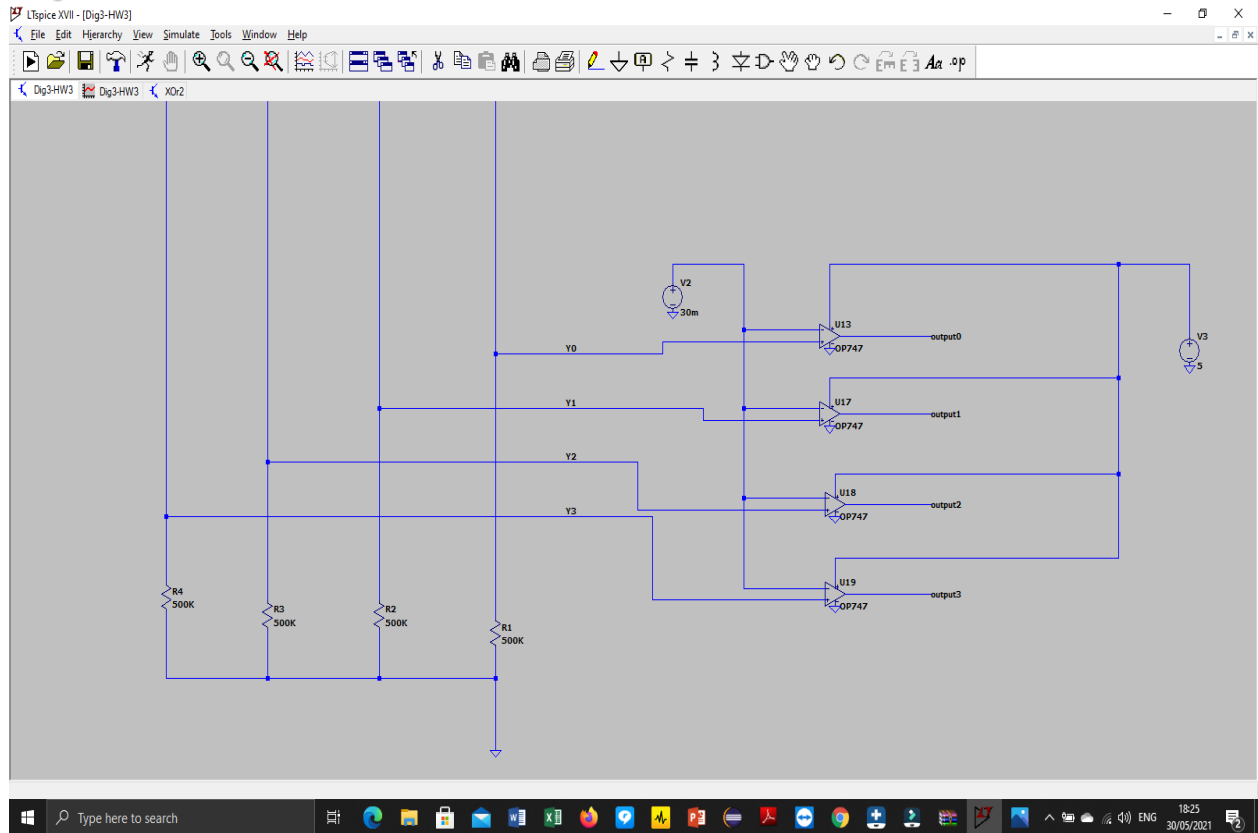Then , we used pull-down resistors to get output correctly , and then amplify output.



Then We RUN ..

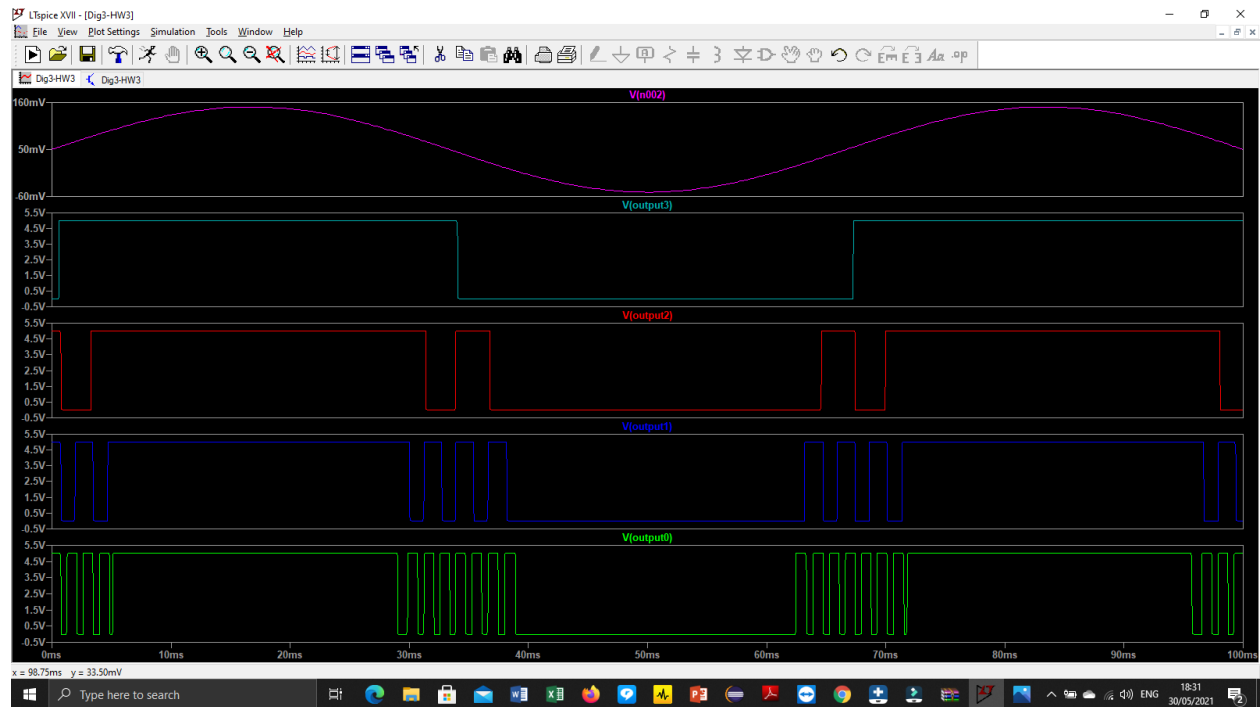

If I would to verify the 10 if it exist or no in curves:

$(10/16) * 100\text{mv} = 62.5\text{mV}$, and then point on the input wave on $Y=62.5\text{mV}$, then the output curves will be :

$V \text{ output3} = \text{High}$

$V \text{ output2} = \text{Low}$

$V \text{ output1} = \text{High}$

$V \text{ output0} = \text{Low}$

- *$V \text{ output 3} : \text{Most Significant Bit.}$*
- *$V \text{ output 0} : \text{Least Significant Bit.}$*

Components

| <i>Component Name</i> | <i>Count</i> |
|--|---------------------|
| <i>Op-Amp's</i> | <i>19</i> |
| <i>Diodes</i> | <i>32</i> |
| <i>CMOS Transistors</i> <i>(we used 15 XOR each XOR</i> <i>Consist of 8 CMOS Transistors)</i> | <i>120</i> |